

VLSI Lab Report

Assignment 2 Annexure 1

BCSE 4th Year 2nd Semester

*Name: **Priti Shaw***

*Roll No. : **001710501076***

*Batch: **A3***


*Submission Date: **06th April 2021***

1. Description


Design 16 X 4 encoder using 4 X 2 encoders using generate statement. Write test bench using loop statements(for and while).

An encoder in digital electronics is a one-hot to binary converter. That is if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. A 16-to-4 encoder has 16 input lines and 4 output lines.

2. Block Diagram

 

3. Circuit Diagram

 

4. Truth table

Input																Output			
i ₁₅	i ₁₄	i ₁₃	i ₁₂	i ₁₁	i ₁₀	i ₉	i ₈	i ₇	i ₆	i ₅	i ₄	i ₃	i ₂	i ₁	i ₀	o ₃	o ₂	o ₁	o ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	1
0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	1	0
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1

5. Entity

```
entity Annexure2 is
    Port ( input : in  STD_LOGIC_VECTOR (15 downto 0);
          output : out STD_LOGIC_VECTOR (3 downto 0));
end Annexure2;
```

6. Architecture

```
architecture Behavioral of Annexure2 is
    component QuestionTwo_Part2 is
        Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
              oo : out STD_LOGIC_VECTOR (1 downto 0));
    end component;
    signal p: std_logic_vector(3 downto 0);

    begin
        p(0) <= input(0) or input(1) or input(2) or input(3);
        p(1) <= input(4) or input(5) or input(6) or input(7);
        p(2) <= input(8) or input(9) or input(10) or input(11);
        p(3) <= input(12) or input(13) or input(14) or input(15);
        c5: QuestionTwo_Part2 port map(p, output(3 downto 2));

        gen1: for k in 0 to 3 generate
            cc: QuestionTwo_Part2 port map(input(((4*k)+3) downto (4*k)),
            output(1 downto 0));
        end generate;
    end Behavioral;
```

7. TestBench

a) Using for loop

```
ENTITY Annexure2_TestBench IS
END Annexure2_TestBench;

ARCHITECTURE behavior OF Annexure2_TestBench IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT Annexure2
```

```

    PORT(
        input : IN  std_logic_vector(15 downto 0);
        output : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;
    --Inputs
    signal input : std_logic_vector(15 downto 0) := (others => '0');
    --Outputs
    signal output : std_logic_vector(3 downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: Annexure2 PORT MAP (
        input => input,
        output => output
    );
    stim_proc: process
        variable j: integer;
    begin
        for j in 0 to 15 loop
            if j=0 then
                input(j)<='1';
                input(15)<='0';
                wait for 1 ps;
            else
                input(j-1)<='0';
                input(j)<='1';
                wait for 1 ps;
            end if;
        end loop;
    end process;
END;

```

b) Using while loop

```

ENTITY Annexure2_TestBench IS
END Annexure2_TestBench;

```


```

ARCHITECTURE behavior OF Annexure2_TestBench IS
    COMPONENT Annexure2
    PORT(
        input : IN  std_logic_vector(15 downto 0);
        output : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;
--Inputs
signal input : std_logic_vector(15 downto 0) := (others => '0');
--Outputs
signal output : std_logic_vector(3 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: Annexure2 PORT MAP (
        input => input,
        output => output
    );
    stim_proc: process
        variable j: integer;
    begin
        j:=0;
        while j<16 loop
            if j=0 then
                input(j)<='1';
                input(15)<='0';
                wait for 1 ps;
            else
                input(j-1)<='0';
                input(j)<='1';
                wait for 1 ps;
            end if;
            j:=j+1;
        end loop;
    end process;
END;

```

8. Timing Diagram

a) Using *For* loop

 

b) Using *While* loop

