

VLSI Lab Report Assignment 2

BCSE 4th Year 2nd Semester

*Name: **Priti Shaw***

*Roll No. : **001710501076***

*Batch: **A3***

*Submission Date: **05th April 2021***

1. Design 2 X 1 Encoder using behavioral level Modelling


Description

An encoder in digital electronics is a one-hot to binary converter. That is if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. A 2-to-1 encoder has 2 input lines and 1 output line.


Truth Table

Input		Output
i_1	i_0	o_0
0	1	0
1	0	1

Block Diagram

 

Circuit Diagram

 

Architecture

a) Using ***if-else*** statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionOne is
    Port ( i : in  STD_LOGIC_VECTOR (1 downto 0);
          o : out  STD_LOGIC);
end QuestionOne;

architecture Behavioral of QuestionOne is

begin
p1:process(i)
    begin
        if i="01" then
            o<='0';
        elsif i="10" then
            o<='1';
        else
            o<='Z';
        end if;
    end process;
end Behavioral;
```

b) Using ***case*** statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionOne_Part2 is
    Port ( i : in  STD_LOGIC_VECTOR (1 downto 0);
          o : out  STD_LOGIC);
end QuestionOne_Part2;

architecture Behavioral of QuestionOne_Part2 is

begin
p2:process(i)
```

```

begin
case i is
    when "01" => o<='0';
    when "10" => o<='1';
    when others => o<='Z';
end case;
end process;
end Behavioral;

```

c) Using **when else** statement

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionOne_Part3 is
    Port ( i : in  STD_LOGIC_VECTOR (1 downto 0);
          o : out  STD_LOGIC);
end QuestionOne_Part3;

architecture Behavioral of QuestionOne_Part3 is

begin
o<= '0' when i<="01" else
    '1' when i<="10" else
    'Z';
end Behavioral;

```

d) Using **select when** statement

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionOne_Part4 is
    Port ( i : in  STD_LOGIC_VECTOR (1 downto 0);
          o : out  STD_LOGIC);
end QuestionOne_Part4;

architecture Behavioral of QuestionOne_Part4 is

begin
with i select
    o<='0' when "01",

```

```
        '1' when "10",  
        'Z' when others;  
end Behavioral;
```

TestBench


```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
  
ENTITY QuestionOne_TestBench IS  
END QuestionOne_TestBench;  
  
ARCHITECTURE behavior OF QuestionOne_TestBench IS  
  
    COMPONENT QuestionOne  
    PORT(  
        i : IN  std_logic_vector(1 downto 0);  
        o : OUT std_logic  
    );  
    END COMPONENT;  
  
    --Inputs  
    signal i : std_logic_vector(1 downto 0) := (others => '0');  
    --Outputs  
    signal o : std_logic;  
  
BEGIN  
    -- Instantiate the Unit Under Test (UUT)  
    uut: QuestionOne PORT MAP (  
        i => i,  
        o => o  
    );  
  
    -- Stimulus process  
    stim_proc: process  
    begin  
        i<="01";  
        wait for 1 ps;  
        i<="10";  
        wait for 1 ps;  
        i<="11";  
        wait for 1 ps;  
    end process;  
END;
```

Timing Diagram


a) Using if-else statement




b) Using case statement

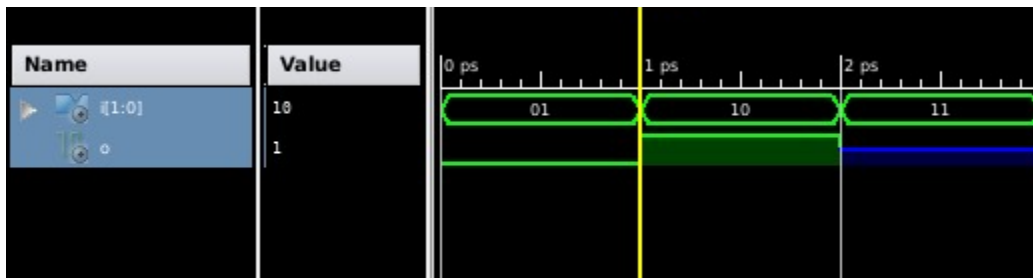

c) Using when else statement

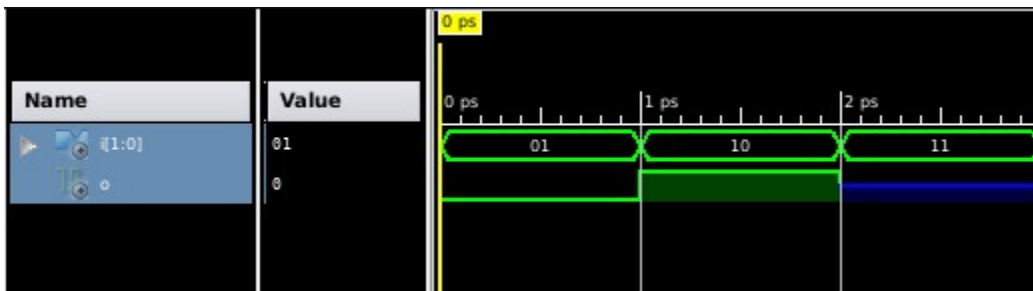

d) Using select when statement

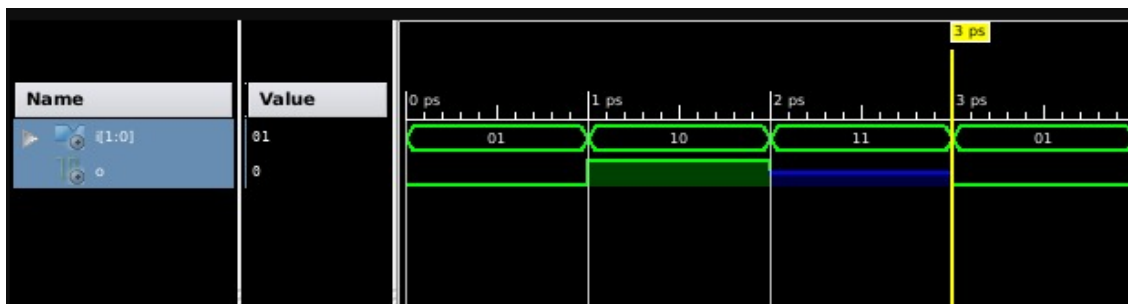


2. Design 4 X 2 Encoder


Description

An encoder in digital electronics is a one-hot to binary converter. That is if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. A 4-to-2 encoder has 4 input lines and 2 output lines.

Block Diagram

 

Circuit Diagram

 

Truth Table

Input				Output	
i3	i2	i1	i0	o1	o0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

Architecture

a) Using Gate level Modelling

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionTwo_Part1 is
    Port ( i : in STD_LOGIC_VECTOR (3 downto 0);
          o : out STD_LOGIC_VECTOR (1 downto 0));
end QuestionTwo_Part1;

architecture Behavioral of QuestionTwo_Part1 is

begin
    o(0) <= i(1) or i(3);
    o(1) <= i(2) or i(3);
end Behavioral;
```


b) Using behavioral Modelling

i) if-else statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionTwo_Part2 is
    Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
          oo : out STD_LOGIC_VECTOR (1 downto 0));
end QuestionTwo_Part2;
architecture Behavioral of QuestionTwo_Part2 is

begin
p1:process(ii)
    begin
        if ii="0001" then
            oo<="00";
        elsif ii="0010" then
            oo<="01";
        elsif ii="0100" then
            oo<="10";
        elsif ii="1000" then
            oo<="11";
        else
            oo<="ZZ";
        end if;
    end process;
end Behavioral;
```

ii) case statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionTwo_Part2_B is
    Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
          oo : out STD_LOGIC_VECTOR (1 downto 0));
end QuestionTwo_Part2_B;

architecture Behavioral of QuestionTwo_Part2_B is

begin
```

```

p2:process(ii)
begin
  case ii is
    when "0001" => oo<="00";
    when "0010" => oo<="01";
    when "0010" => oo<="10";
    when "1000" => oo<="11";
    when others => oo<="ZZ";
  end case;
end process;
end Behavioral;

```

iii) when else statement

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionTwo_Part2_C is
  Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
        oo : out STD_LOGIC_VECTOR (1 downto 0));
end QuestionTwo_Part2_C;

architecture Behavioral of QuestionTwo_Part2_C is

begin
  oo<="00" when ii<="0001" else
    "01" when ii<="0010" else
    "10" when ii<="0100" else
    "11" when ii<="1000" else
    "ZZ";
end Behavioral;

```

iv) select when statement

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionTwo_Part2_D is
  Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
        oo : out STD_LOGIC_VECTOR (1 downto 0));
end QuestionTwo_Part2_D;

```

```

architecture Behavioral of QuestionTwo_Part2_D is

begin
with ii select
    oo<="00" when "0001",
        "01" when "0010",
        "10" when "0100",
        "11" when "1000",
        "ZZ" when others;
end Behavioral;

```

Test Bench

a) Using Gate level Modelling

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY QuestionTwo_Part1_TestBench IS
END QuestionTwo_Part1_TestBench;

ARCHITECTURE behavior OF QuestionTwo_Part1_TestBench IS
    COMPONENT QuestionTwo_Part1
    PORT(
        i : IN  std_logic_vector(3 downto 0);
        o : OUT std_logic_vector(1 downto 0)
    );
    END COMPONENT;
    --Inputs
    signal i : std_logic_vector(3 downto 0) := (others => '0');
    --Outputs
    signal o : std_logic_vector(1 downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionTwo_Part1 PORT MAP (
        i => i,
        o => o
    );
    -- Stimulus process

```

```

stim_proc: process
begin
    i<="0001";
    wait for 1 ps;
    i<="0010";
    wait for 1 ps;
    i<="0100";
    wait for 1 ps;
    i<="1000";
    wait for 1 ps;
end process;
END;

```

b) Using behavioral Modelling - if-else statement

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY QuestionTwo_Part2_TestBench IS
END QuestionTwo_Part2_TestBench;

ARCHITECTURE behavior OF QuestionTwo_Part2_TestBench IS

    COMPONENT QuestionTwo_Part2
    PORT(
        ii : IN  std_logic_vector(3 downto 0);
        oo : OUT std_logic_vector(1 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal ii : std_logic_vector(3 downto 0) := (others => '0');
    --Outputs
    signal oo : std_logic_vector(1 downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionTwo_Part2 PORT MAP (
        ii => ii,
        oo => oo
    );

```

```

-- Stimulus process
stim_proc: process
begin
    ii<="0001";
    wait for 1 ps;
    ii<="0010";
    wait for 1 ps;
    ii<="0100";
    wait for 1 ps;
    ii<="1000";
    wait for 1 ps;
    ii<="1100";
    wait for 1 ps;
end process;
END;

```


Timing Diagram

a) Gate level Modelling




b) Behavioral Level Modelling


i) if-else statement

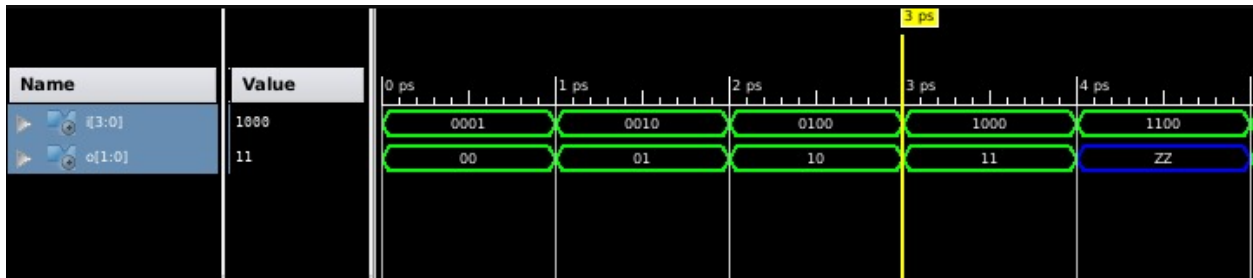


ii) Case statement

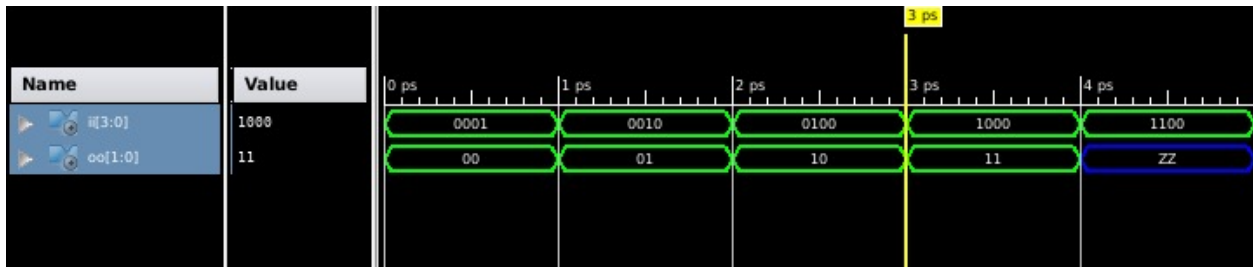

iii) When else statement

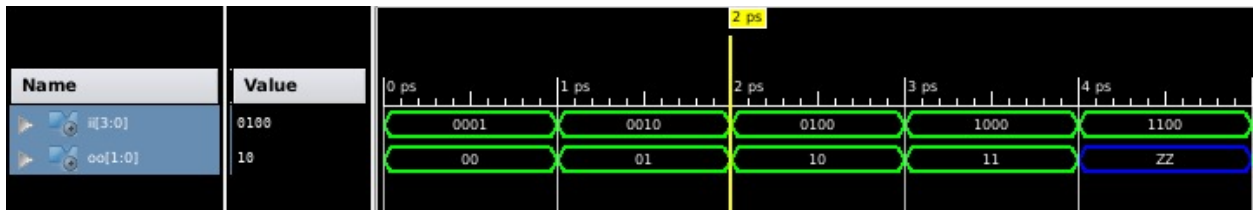

iv) Switch when statement

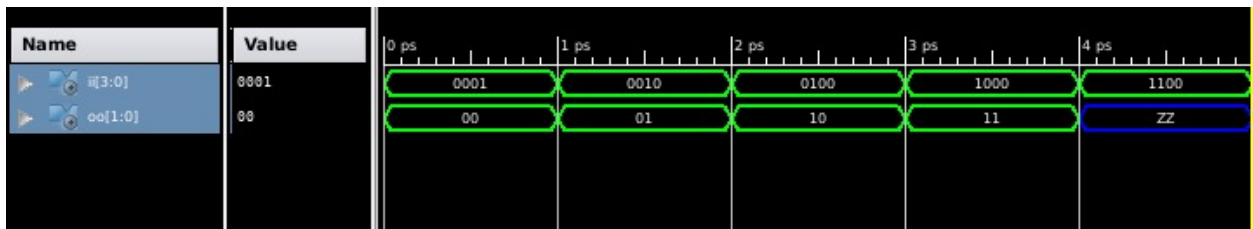


3. Design 8 X 3 Encoder.


Description

An encoder in digital electronics is a one-hot to binary converter. That is if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. An 8-to-3 encoder has 8 input lines and 3 output lines.

Block Diagram

 

Circuit Diagram

 

Truth Table

Input								Output		
i7	i6	i5	i4	i3	i2	i1	i0	o2	o1	o0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

Architecture

a) Using Gate level Modelling

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionThree_Part1 is
    Port ( i : in  STD_LOGIC_VECTOR (7 downto 0);
          o : out STD_LOGIC_VECTOR (2 downto 0));
end QuestionThree_Part1;

architecture Behavioral of QuestionThree_Part1 is

begin
    o(2)<=i(7) or i(6) or i(5) or i(4);
    o(1)<=i(7) or i(6) or i(3) or i(2);
    o(0)<=i(7) or i(5) or i(3) or i(1);
end Behavioral;
```


b) Using Behavioral Modelling - if-else statement

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionThree_Part2 is
    Port ( i : in  STD_LOGIC_VECTOR (7 downto 0);
          o : out STD_LOGIC_VECTOR (2 downto 0));
end QuestionThree_Part2;

architecture Behavioral of QuestionThree_Part2 is

begin
    p1:process(i)
    begin
        if i="00000001" then
            o<="000";
        elsif i="00000010" then
            o<="001";
        elsif i="00000100" then
            o<="010";
        elsif i="00001000" then
            o<="011";
        elsif i="00010000" then
            o<="100";
        elsif i="00100000" then
            o<="101";
        elsif i="01000000" then
            o<="110";
        elsif i="10000000" then
            o<="111";
        else
            o<="ZZZ";
        end if;
    end process;
end Behavioral;
```

Test Bench

a) Using Gate level Modelling

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY QuestionThree_Part1_TestBench IS
END QuestionThree_Part1_TestBench;

ARCHITECTURE behavior OF QuestionThree_Part1_TestBench IS
    COMPONENT QuestionThree_Part1
    PORT(
        i : IN  std_logic_vector(7 downto 0);
        o : OUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal i : std_logic_vector(7 downto 0) := (others => '0');
    --Outputs
    signal o : std_logic_vector(2 downto 0);

BEGIN
    uut: QuestionThree_Part1 PORT MAP (
        i => i,
        o => o
    );
    stim_proc: process
    begin
        i<="00000001";
        wait for 1 ps;
        i<="00000010";
        wait for 1 ps;
        i<="00000100";
        wait for 1 ps;
        i<="00001000";
        wait for 1 ps;
        i<="00010000";
        wait for 1 ps;
        i<="00100000";
```

```

        wait for 1 ps;
        i<="01000000";
        wait for 1 ps;
        i<="10000000";
        wait for 1 ps;
    end process;
END;

```

b) Using behavioral Modelling - if-else statement

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY QuestionThree_Part2_TestBench IS
END QuestionThree_Part2_TestBench;

ARCHITECTURE behavior OF QuestionThree_Part2_TestBench IS

    COMPONENT QuestionThree_Part2
    PORT(
        i : IN  std_logic_vector(7 downto 0);
        o : OUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal i : std_logic_vector(7 downto 0) := (others => '0');
    --Outputs
    signal o : std_logic_vector(2 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionThree_Part2 PORT MAP (
        i => i,
        o => o
    );

    -- Stimulus process
    stim_proc: process
    begin
        i<="00000001";
        wait for 1 ps;
        i<="00000010";
        wait for 1 ps;
    end process;

```


```

i<="00000100";
wait for 1 ps;
i<="00001000";
wait for 1 ps;
i<="00010000";
wait for 1 ps;
i<="00100000";
wait for 1 ps;
i<="01000000";
wait for 1 ps;
i<="10000000";
wait for 1 ps;
i<="10100010";
wait for 1 ps;
end process;
END;


```

Timing Diagram

a) For Gate level Modelling

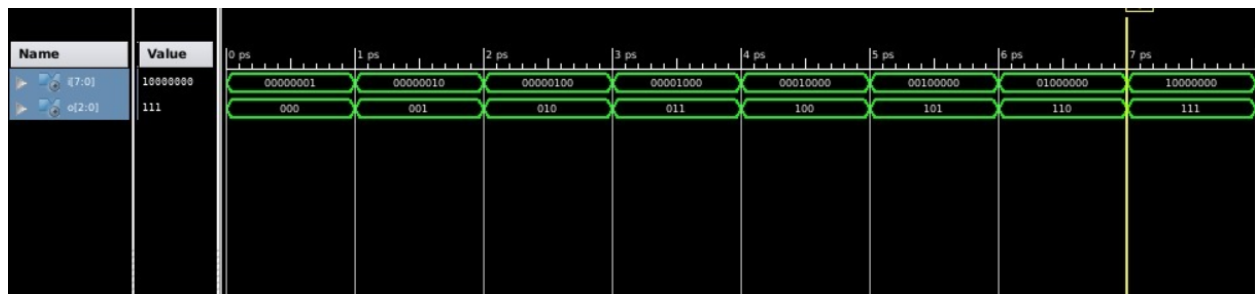

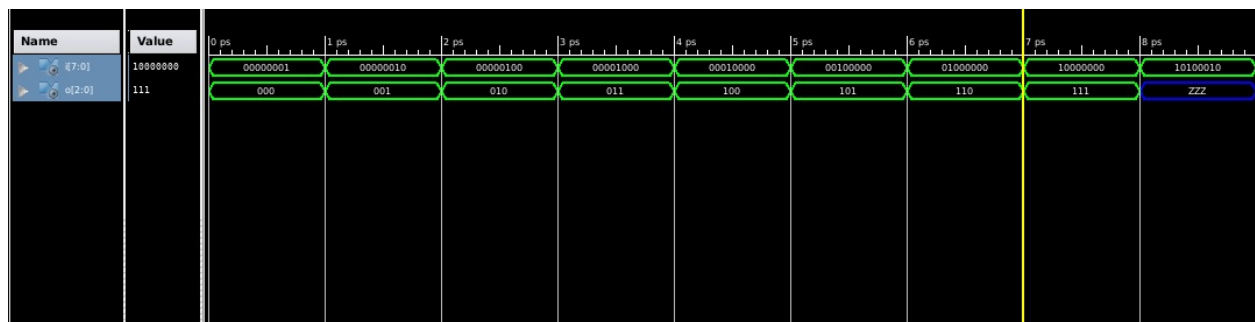b) For behavioral Modelling - if-else statement



[illegible]

Architecture

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionFour is
    Port ( iii : in  STD_LOGIC_VECTOR (7 downto 0);
          ooo : out STD_LOGIC_VECTOR (2 downto 0));
end QuestionFour;

architecture Behavioral of QuestionFour is
    component QuestionTwo_Part2 is
        Port ( ii : in STD_LOGIC_VECTOR (3 downto 0);
              oo : out STD_LOGIC_VECTOR (1 downto 0));
    end component;

    component QuestionOne is
        Port ( i : in STD_LOGIC_VECTOR (1 downto 0);
              o : out STD_LOGIC );
    end component;

    signal a,b,p: STD_LOGIC_VECTOR(1 downto 0);
    signal q: STD_LOGIC;

begin
    c1: QuestionTwo_Part2 port map(iii(3 downto 0), a);
    c2: QuestionTwo_Part2 port map(iii(7 downto 4), b);
    c3: QuestionOne port map(p, q);
    p(0)<= iii(0) or iii(1) or iii(2) or iii(3);
    p(1)<= iii(4) or iii(5) or iii(6) or iii(7);
    p1:process(iii,p,q,a,b)
        begin
            if iii(7 downto 4)="0000" then
                ooo<= q & a;
            elsif iii(3 downto 0)="0000" then
                ooo<= q & b;
            else
                ooo<= "ZZZ";
            end if;
        end process;
end Behavioral;
```

Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY QuestionFour_TestBench IS
END QuestionFour_TestBench;
ARCHITECTURE behavior OF QuestionFour_TestBench IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT QuestionFour
    PORT(
        iii : IN  std_logic_vector(7 downto 0);
        ooo : OUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal iii : std_logic_vector(7 downto 0) := (others => '0');

    --Outputs
    signal ooo : std_logic_vector(2 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionFour PORT MAP (
        iii => iii,
        ooo => ooo
    );


    -- Stimulus process
    stim_proc: process
    begin
        iii<="00000001";
        wait for 1 ps;
        iii<="00000010";
        wait for 1 ps;
        iii<="00000100";
        wait for 1 ps;
        iii<="00001000";
        wait for 1 ps;
```

```

    iii<="00010000";
    wait for 1 ps;
    iii<="00100000";
    wait for 1 ps;
    iii<="01000000";
    wait for 1 ps;
    iii<="10000000";
    wait for 1 ps;
    iii<="10000010";
    wait for 1 ps;
end process;
END;

```

Timing Diagram

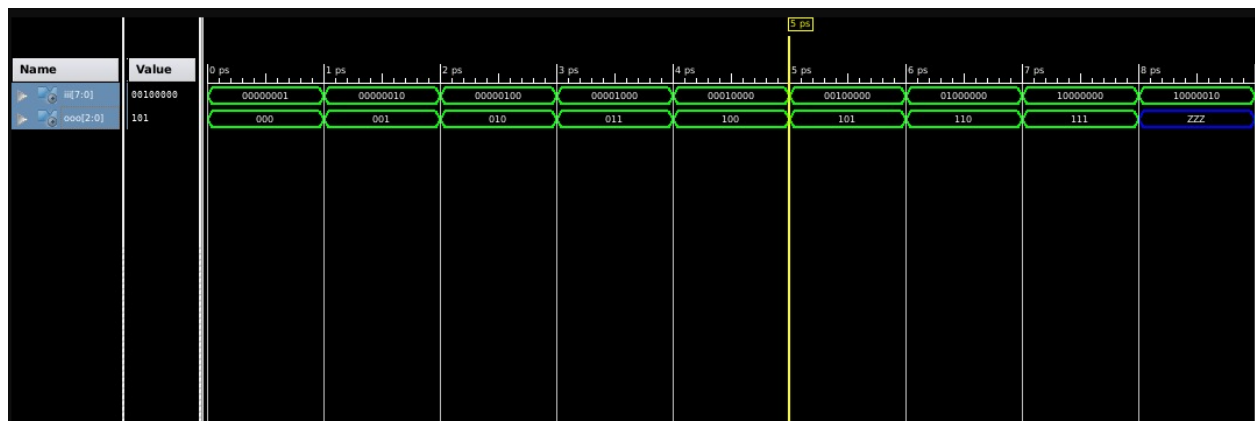


5. Design a 16 X 4 encoder using 4 X 2 encoders only.


Description

An encoder in digital electronics is a one-hot to binary converter. That is if there are 2^n input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n-bit output lines. A 16-to-4 encoder has 16 input lines and 4 output lines.

Block Diagram

 

Circuit Diagram

 

Truth Table

Input																Output			
i ₁₅	i ₁₄	i ₁₃	i ₁₂	i ₁₁	i ₁₀	i ₉	i ₈	i ₇	i ₆	i ₅	i ₄	i ₃	i ₂	i ₁	i ₀	o ₃	o ₂	o ₁	o ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	1	1
0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0
0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	1	0	1
0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	1	0	0
0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	1	1	1
0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	1	1	0
0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	1	0	0	1
0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	1	0	1	1
0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	1	0	1	0
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	1
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0

Architecture

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity QuestionFive is
    Port ( i : in  STD_LOGIC_VECTOR (15 downto 0);
          o : out  STD_LOGIC_VECTOR (3 downto 0));
end QuestionFive;

architecture Behavioral of QuestionFive is

    component QuestionTwo_Part2 is
        Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
              oo : out STD_LOGIC_VECTOR (1 downto 0));
    end component;

    signal p: STD_LOGIC_VECTOR(3 downto 0);
    signal a,b,c,d,q: STD_LOGIC_VECTOR(1 downto 0);

begin
    c1: QuestionTwo_Part2 port map(i(3 downto 0), a);
    c2: QuestionTwo_Part2 port map(i(7 downto 4), b);
    c3: QuestionTwo_Part2 port map(i(11 downto 8), c);
    c4: QuestionTwo_Part2 port map(i(15 downto 12), d);
    c5: QuestionTwo_Part2 port map(p, q);
    p(0)<= i(3) or i(2) or i(1) or i(0);
    p(1)<= i(7) or i(6) or i(5) or i(4);
    p(2)<= i(11) or i(10) or i(9) or i(8);
    p(3)<= i(15) or i(14) or i(13) or i(12);
    p1:process(i,p,q,a,b,c,d)
        begin
            if i(7 downto 4)="0000" and i(11 downto 8)="0000" and i(15 downto 12)="0000" then
                o<= q & a;
            elsif i(3 downto 0)="0000" and i(11 downto 8)="0000" and i(15 downto 12)="0000" then
                o<= q & b;
            elsif i(3 downto 0)="0000" and i(7 downto 4)="0000" and i(15 downto 12)="0000" then
                o<= q & c;
            elsif i(3 downto 0)="0000" and i(7 downto 4)="0000" and i(11 downto 8)="0000" then
```

```

        o<= q & d;
    else
        o<="ZZZZ";
    end if;
end process;
end Behavioral;

```

Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY QuestionFive_TestBench IS
END QuestionFive_TestBench;

ARCHITECTURE behavior OF QuestionFive_TestBench IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT QuestionFive
    PORT(
        i : IN  std_logic_vector(15 downto 0);
        o : OUT std_logic_vector(3  downto 0)
    );
    END COMPONENT;
    --Inputs
    signal i : std_logic_vector(15 downto 0) := (others => '0');
    --Outputs
    signal o : std_logic_vector(3  downto 0);

BEGIN
    uut: QuestionFive PORT MAP (
        i => i,
        o => o
    );
    stim_proc: process
    begin
        i<="0000000000000001";
        wait for 1 ps;
        i<="0000000000000010";
        wait for 1 ps;
        i<="0000000000000100";
        wait for 1 ps;
    end process;

```

```

        i<="0000000000001000";
        wait for 1 ps;
        i<="0000000000010000";
        wait for 1 ps;
        i<="0000000000100000";
        wait for 1 ps;
        i<="0000000001000000";
        wait for 1 ps;
        i<="0000000010000000";
        wait for 1 ps;
        i<="0000000100000000";
        wait for 1 ps;
        i<="0000001000000000";
        wait for 1 ps;
        i<="0000010000000000";
        wait for 1 ps;
        i<="0000100000000000";
        wait for 1 ps;
        i<="0001000000000000";
        wait for 1 ps;
        i<="0010000000000000";
        wait for 1 ps;
        i<="0100000000000000";
        wait for 1 ps;
        i<="1000000000000000";
        wait for 1 ps;
        i<="1000000010000010";
        wait for 1 ps;
    end process;
END;

```

Timing Diagram

