

VLSI Lab Report

Assignment 3 Annexure 1

BCSE 4th Year 2nd Semester

*Name: **Priti Shaw***

*Roll No. : **001710501076***


*Batch: **A3***

1. Description


Design 4 X 16 decoder using 2 X 4 decoders using generate statement. Write a test bench using a behavioral statement.

A decoder is a combinational circuit that has N input lines and a maximum of 2^N output lines. One of these outputs will be active high based on the combination of inputs present when the decoder is enabled. That means the decoder detects a particular code. A 4 to 16 decoder has 4 input lines and 16 output lines. An enable input is provided to switch the decoder on and off.

2. Block Diagram

 

3. Circuit Diagram

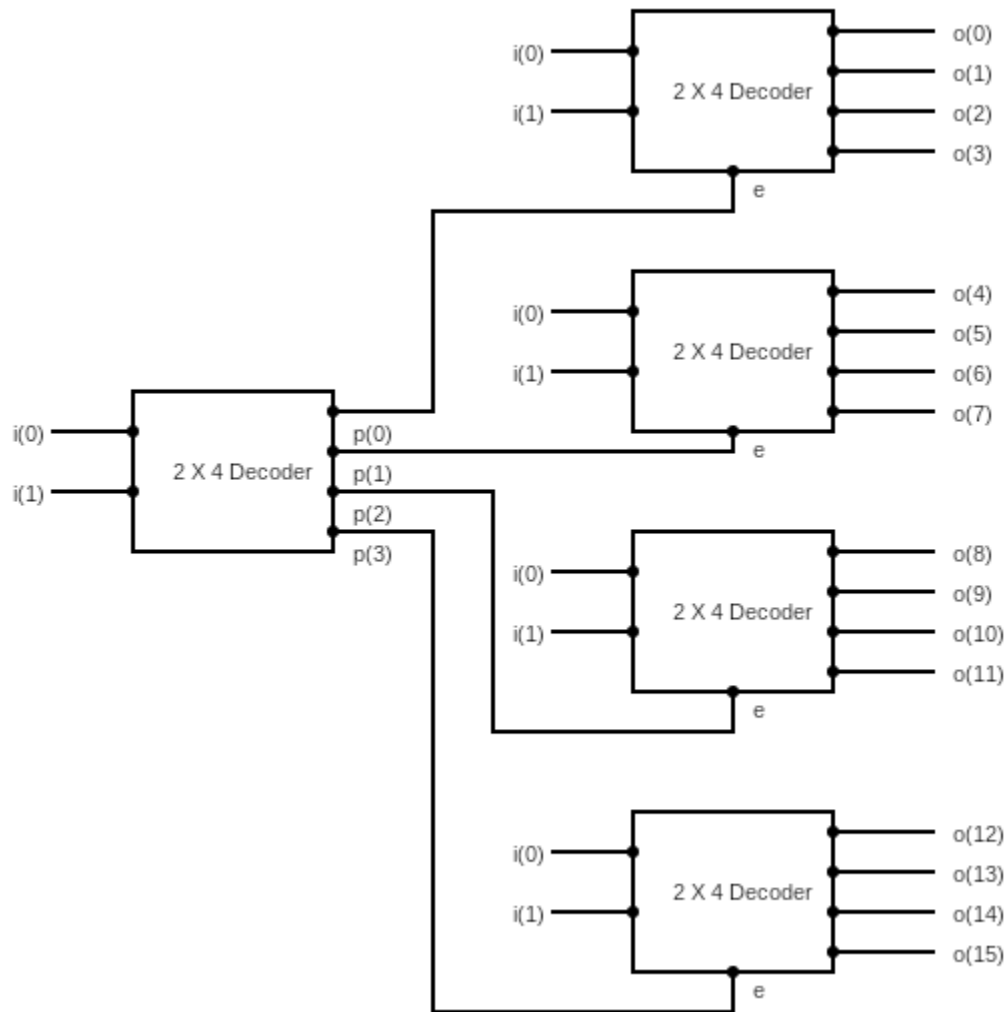

4. Entity

```
entity Annexure1 is
    Port ( enable : in  STD_LOGIC;
          input  : in  STD_LOGIC_VECTOR (3 downto 0);
          output : out  STD_LOGIC_VECTOR (15 downto 0));
end Annexure1;
```

5. Truth Table

[illegible]

6. Architecture

```
architecture Behavioral of Annexure1 is

component QuestionTwo_PartB_one is
    Port ( ee : in  STD_LOGIC;
          ii : in  STD_LOGIC_VECTOR (1 downto 0);
          oo : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal p: STD_LOGIC_VECTOR(3 downto 0);

begin
c4: QuestionTwo_PartB_one port map(enable, input(3 downto 2), p);
gen1: for k in 0 to 3 generate
    cc: QuestionTwo_PartB_one port map(p(k), input(1 downto 0),
output(((4*k)+3) downto (4*k)));
end generate;
end Behavioral;
```

7. TestBench

```
ENTITY Annexure1_TestBench IS
END Annexure1_TestBench;

ARCHITECTURE behavior OF Annexure1_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT Annexure1
    PORT(
        enable : IN  std_logic;
        input  : IN  std_logic_vector(3 downto 0);
        output : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal enable : std_logic := '0';
    signal input  : std_logic_vector(3 downto 0) := (others => '0');

    --Outputs
    signal output : std_logic_vector(15 downto 0);
```

```

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: Annexure1 PORT MAP (
        enable => enable,
        input => input,
        output => output
    );
    -- Stimulus process
    stim_proc: process
        variable k,j,a:integer;
    begin
        if enable='0' then
            enable<='1';
        elsif enable='1' then
            enable<='0';
        end if;
        for k in 0 to 15 loop
            j:=k;
            a:=0;
            while a<4 loop
                if (j rem 2)=0 then
                    input(a)<='0';
                elsif (j rem 2)=1 then
                    input(a)<='1';
                end if;
                j:=j/2;
                a:=a+1;
            end loop;
            wait for 1 ps;
        end loop;
    end process;
END;

```

8. Timing Diagram

