

VLSI Lab Report Assignment 6

BCSE 4th Year 2nd Semester

*Name: **Priti Shaw***

*Roll No. : **001710501076***

*Batch: **A3***


1. 2 X 1 Multiplexer

Description

Implement a 2X1 multiplexer using gate level modelling.

2 X 1 Multiplexer takes two inputs and using one select line, it selects any one of the two input lines and gives it as output. A bit binary number formed by the select lines determine the index of the input line which will be selected.

Block Diagram

 

Truth Table

s	o_0
0	i_0
1	i_1

Entity

```
entity twoCrossOneMux is
    Port ( i : in  STD_LOGIC_VECTOR (1 downto 0);
           s : in  STD_LOGIC;
           o : out STD_LOGIC);
end twoCrossOneMux;
```

Architecture


```
architecture Behavioral of twoCrossOneMux is

begin
  p1:process(i,s)
    variable oo:std_logic;
    begin
      proc: twoCrossOneMuxProcedure(i(1 downto 0),s,oo);
      o<=oo;
    end process;
end Behavioral;
```

Procedure of 2X1 Multiplexer in Package

```
procedure twoCrossOneMuxProcedure(i: in std_logic_vector;s:in std_logic;o:
out std_logic) is
  variable ii: std_logic_vector(1 downto 0);
  begin
    ii(0):= not(s) and i(0);
    ii(1):= s and i(1);
    o:= ii(0) or ii(1);
  end procedure;
```

Timing Diagram

 


2. 4 X 1 Multiplexer

Description

Implement a 4X1 multiplexer using gate level modelling.

4 X 1 Multiplexer takes four inputs and using two select lines, it selects any one of the four input lines and gives it as output. The two bit binary number formed by the select lines determine the index of the input line which will be selected.

Block Diagram

 

Truth Table

s_1	s_0	o_0
0	0	i_0
0	1	i_1
1	0	i_2
1	1	i_3

Entity

```
entity fourCrossOneMux is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
          s : in  STD_LOGIC_VECTOR (1 downto 0);
          o : out  STD_LOGIC);
end fourCrossOneMux;
```

Architecture

```
architecture Behavioral of fourCrossOneMux is

begin
    p1:process(i,s)
        variable oo:std_logic;
        begin
            proc: fourCrossOneMuxProcedure(i(3 downto 0),s(1 downto 0),oo);
            o<=oo;
        end process;
    end Behavioral;
```

Procedure of 4 X 1 Multiplexer in Package

```
procedure fourCrossOneMuxProcedure(i: in std_logic_vector;s:in
std_logic_vector;o: out std_logic) is
    variable ii: std_logic_vector(3 downto 0);
    begin
        ii(0):= not(s(1)) and not(s(0)) and i(0);
        ii(1):= not(s(1)) and s(0) and i(1);
        ii(2):= s(1) and not(s(0)) and i(2);
        ii(3):= s(1) and s(0) and i(3);
        o:= ii(0) or ii(1) or ii(2) or ii(3);
    end procedure;
```

TestBench


```
stim_proc: process
    variable k:integer;
    variable binary:std_logic_vector(1 downto 0);
    begin
        for k in 0 to 3 loop
            prock: decimalToBinaryProcedure(k,2,binary(1 downto
0));

            s(1 downto 0)<=binary(1 downto 0);

            i(3 downto 0)<=(others=>'0');
            i(k)<='1';
            wait for 1 ps;

            i(3 downto 0)<=(others=>'1');
            i(k)<='0';
            wait for 1 ps;
        end loop;
    end process;
END;
```

Timing Diagram

 


3. 8 X 1 Multiplexer using 4 X 1 and 2 X 1 multiplexer

Description

Implement a 8X1 multiplexer using 4X1 multiplexer and 2X1 multiplexer.

8 X 1 Multiplexer takes eight inputs and using three select lines, it selects any one of the eight input lines and gives it as output. The three bit binary number formed by the three select lines determine the index of the input line which will be selected.


Block Diagram

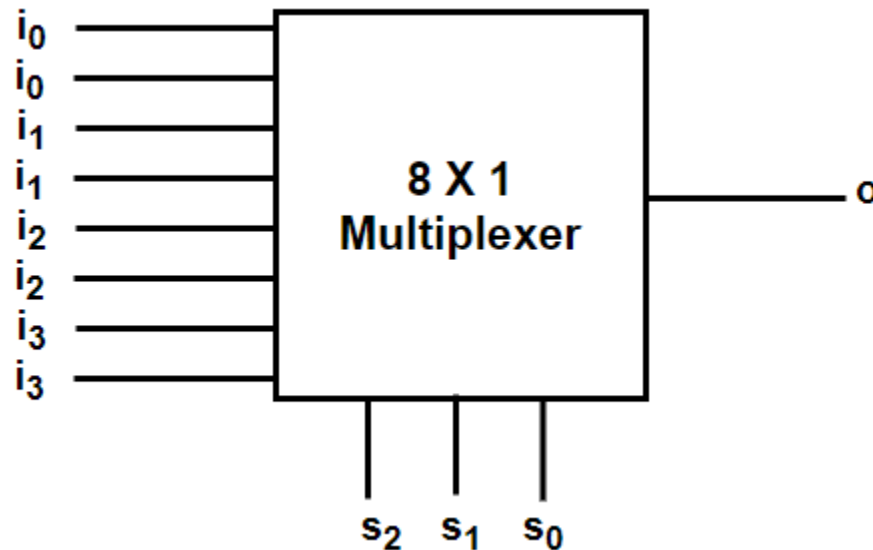

Entity

```
entity eightCrossOneMux is
    Port ( ii : in  STD_LOGIC_VECTOR (7 downto 0);
          ss : in  STD_LOGIC_VECTOR (2 downto 0);
          o : out  STD_LOGIC);
end eightCrossOneMux;
```

Circuit Diagram

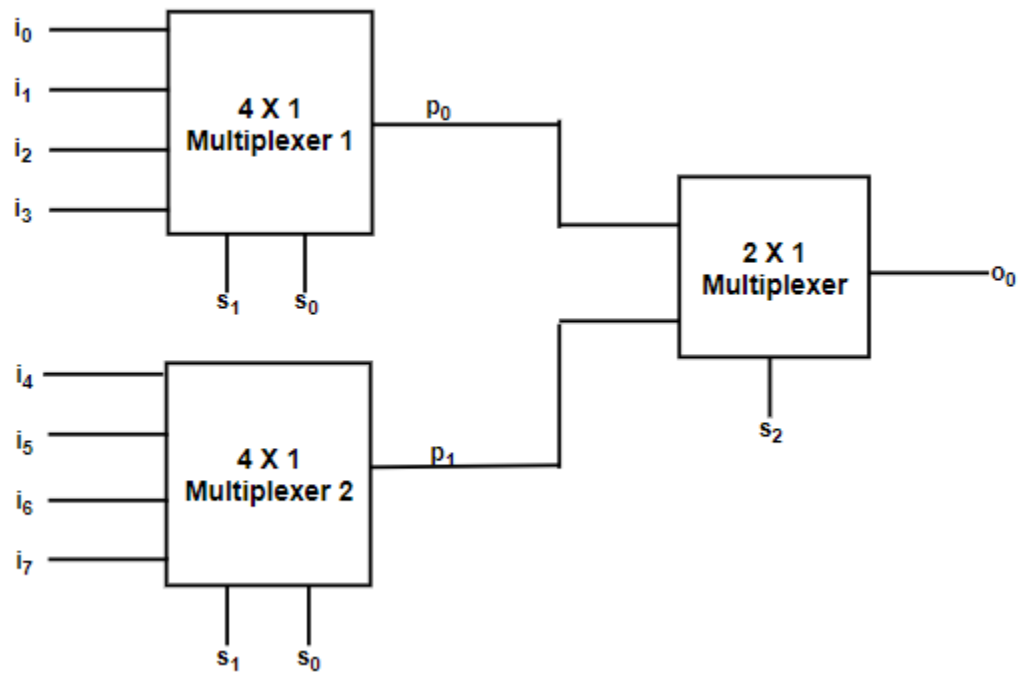

Truth Table

s_2	s_1	s_0	o_0
0	0	0	i_0
0	0	1	i_1
0	1	0	i_2
0	1	1	i_3
1	0	0	i_4
1	0	1	i_5
1	1	0	i_6
1	1	1	i_7

Architecture

```
architecture Behavioral of eightCrossOneMux is

begin
  p1:process(ii,ss)
  variable oo:std_logic;
  begin
    procc: eightCrossOneMuxProcedure(ii(7 downto 0),ss(2 downto 0),oo);
    o<=oo;
  end process;

end Behavioral;
```

Procedure of 8 X 1 Multiplexer in Package

```
procedure eightCrossOneMuxProcedure(i: in std_logic_vector; s: in
std_logic_vector; o: out std_logic) is
  variable p: std_logic_vector(1 downto 0);
  variable ii: std_logic_vector(3 downto 0);
  variable ss: std_logic_vector(1 downto 0);
  variable k: integer;
  begin
    for k in 0 to 1 loop
      ii(3 downto 0) := i(((4*k)+3) downto (4*k));
      ss(1 downto 0) := s(1 downto 0);
      prock: fourCrossOneMuxProcedure(ii(3 downto 0),ss(1 downto
0),p(k));
    end loop;
    procc: twoCrossOneMuxProcedure(p(1 downto 0),s(2),o);
  end procedure;
```


TestBench

```
stim_proc: process
    variable k:integer;
    variable binary:std_logic_vector(2 downto 0);
begin
    for k in 0 to 7 loop
        prock: decimalToBinaryProcedure(k,3,binary(2 downto 0));
        ss(2 downto 0)<=binary(2 downto 0);

        ii(7 downto 0)<=(others=>'0');
        ii(k)<='1';
        wait for 1 ps;

        ii(7 downto 0)<=(others=>'1');
        ii(k)<='0';
        wait for 1 ps;
    end loop;
end process;
END;
```

Timing Diagram

 


4. 16 X 1 Multiplexer using 8 X 1 and 2 X 1 multiplexer

Description

Implement a 16X1 multiplexer using 8X1 multiplexer and 2X1 multiplexer.

16X1 Multiplexer takes sixteen inputs and using four select lines, it selects any one of the sixteen input lines and gives it as output. The four bit binary number formed by the four select lines determine the index of the input line which will be selected.

Block Diagram

 


Entity

```
entity sixteenCrossOneMux82 is
    Port ( i : in  STD_LOGIC_VECTOR (15 downto 0);
          s : in  STD_LOGIC_VECTOR (3 downto 0);
          o : out  STD_LOGIC);
end sixteenCrossOneMux82;
```

Truth Table

s_3	s_2	s_1	s_0	o_0
0	0	0	0	i_0
0	0	0	1	i_1
0	0	1	0	i_2
0	0	1	1	i_3
0	1	0	0	i_4
0	1	0	1	i_5
0	1	1	0	i_6
0	1	1	1	i_7
1	0	0	0	i_8
1	0	0	1	i_9
1	0	1	0	i_{10}
1	0	1	1	i_{11}
1	1	0	0	i_{12}
1	1	0	1	i_{13}
1	1	1	0	i_{14}
1	1	1	1	i_{15}

Circuit Diagram

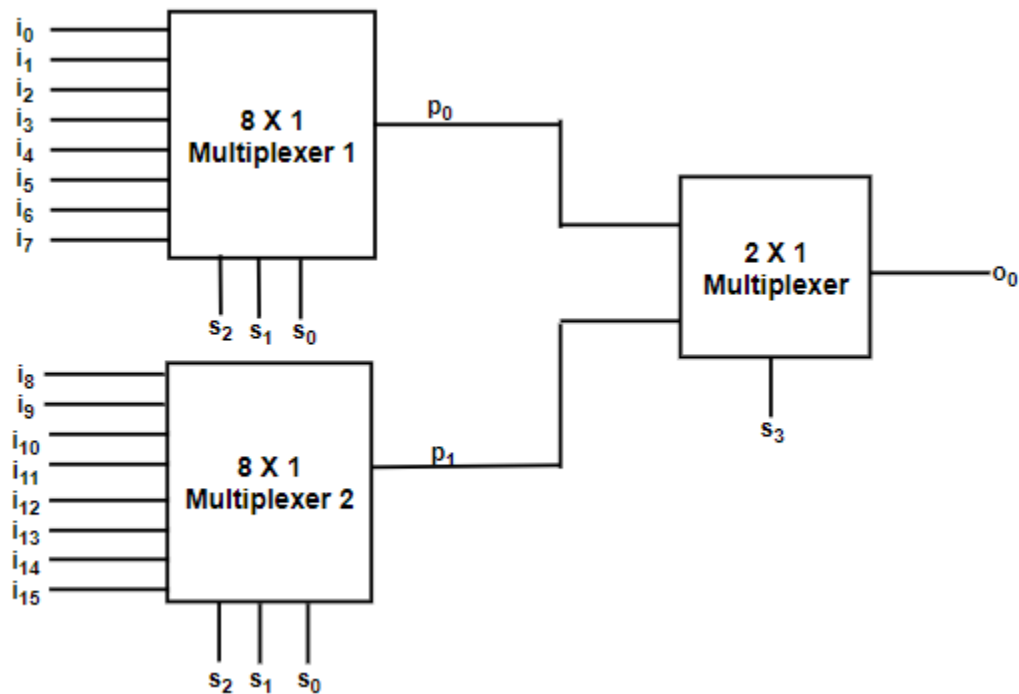

Architecture

```
architecture Behavioral of sixteenCrossOneMux82 is
begin
  process(i, s)
    variable oo: STD_LOGIC;
    begin
      sixteenCrossOneMuxUsing82Procedure(i,s,oo);
      o<=oo;
    end process;
end Behavioral;
```

Procedure of 16 X 1 Multiplexer in Package

```
procedure sixteenCrossOneMuxUsing82Procedure(i: in std_logic_vector;s:in
std_logic_vector;o: out std_logic) is
  variable ss:std_logic_vector(2 downto 0);
  variable p:std_logic_vector(1 downto 0);
  variable a:std_logic_vector(7 downto 0);
  variable k:integer;
begin
  for k in 0 to 1 loop
```

```

        a:=i(8*k+7 downto 8*k);
        ss:=s(2 downto 0);
        eightCrossOneMuxProcedure(a,ss,p(k));
    end loop;
    twoCrossOneMuxProcedure(p,s(3),o);
end procedure;

```

TestBench

```

stim_proc: process
    variable k:integer;
    variable binary:std_logic_vector(3 downto 0);
begin
    for k in 0 to 15 loop
        prock: decimalToBinaryProcedure(k,4,binary(3 downto 0));
        s(3 downto 0)<=binary(3 downto 0);

        i(15 downto 0)<=(others=>'0');
        i(k)<='1';
        wait for 1 ps;

        i(15 downto 0)<=(others=>'1');
        i(k)<='0';
        wait for 1 ps;
    end loop;
end process;

```

Timing Diagram




5. 16 X 1 Multiplexer using 4 X 1 multiplexer

Description

Implement a 16X1 multiplexer using a 4X1 multiplexer only.

16X1 Multiplexer takes sixteen inputs and using four select lines, it selects any one of the sixteen input lines and gives it as output. The four bit binary number formed by the four select lines determine the index of the input line which will be selected.

Block Diagram

 


Entity

```
entity sixteenCrossOneMux is
    Port ( i : in  STD_LOGIC_VECTOR (15 downto 0);
          s : in  STD_LOGIC_VECTOR(3 downto 0);
          o : out STD_LOGIC);
end sixteenCrossOneMux;
```

Truth Table

S₃	S₂	S₁	S₀	O₀
0	0	0	0	i₀
0	0	0	1	i₁
0	0	1	0	i₂
0	0	1	1	i₃
0	1	0	0	i₄
0	1	0	1	i₅
0	1	1	0	i₆
0	1	1	1	i₇
1	0	0	0	i₈
1	0	0	1	i₉
1	0	1	0	i₁₀
1	0	1	1	i₁₁
1	1	0	0	i₁₂
1	1	0	1	i₁₃
1	1	1	0	i₁₄
1	1	1	1	i₁₅

Circuit Diagram

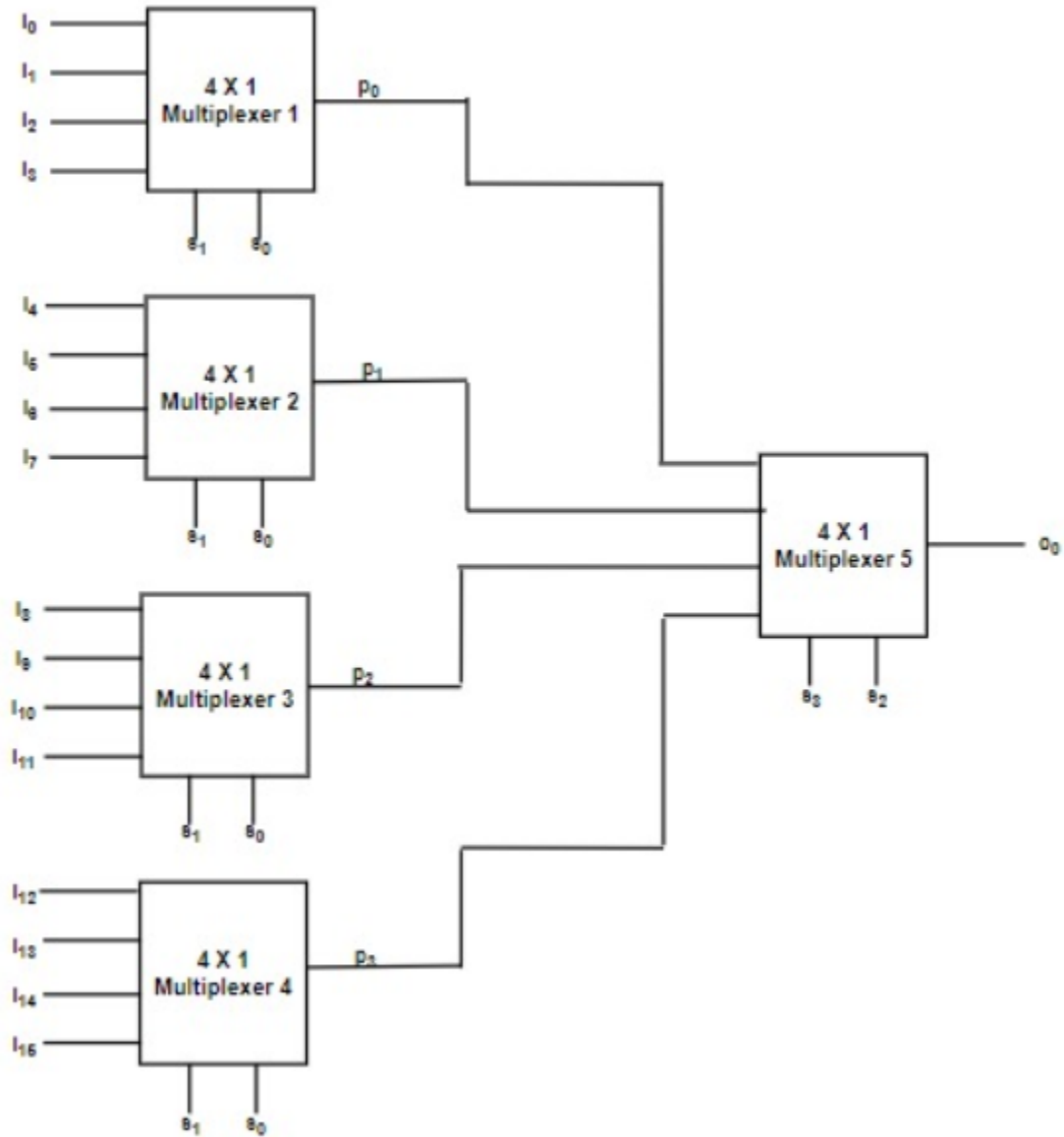

Architecture

```
architecture Behavioral of sixteenCrossOneMux is
begin
    process(i, s)
        variable oo: STD_LOGIC;
        begin
            sixteenCrossOneMuxProcedure(i,s,oo);
            o<=oo;
        end process;
end Behavioral;
```

Procedure of 16 X 1 Multiplexer in Package

```
procedure sixteenCrossOneMuxProcedure(i: in std_logic_vector; s: in
std_logic_vector; o: out std_logic) is
    variable ss: std_logic_vector(1 downto 0);
    variable a, p: std_logic_vector(3 downto 0);
    begin
        for k in 0 to 3 loop
            a := i(4*k+3 downto 4*k);
            ss := s(1 downto 0);
            fourCrossOneMuxProcedure(a, ss, p(k));
        end loop;
        ss := s(3 downto 2);
        fourCrossOneMuxProcedure(p, ss, o);
    end procedure;
```

TestBench

```
stim_proc: process
    variable k: integer;
    variable binary: std_logic_vector(3 downto 0);
    begin
        for k in 0 to 15 loop
            prock: decimalToBinaryProcedure(k, 4, binary(3 downto 0));
            s(3 downto 0) <= binary(3 downto 0);

            i(15 downto 0) <= (others => '0');
            i(k) <= '1';
            wait for 1 ps;

            i(15 downto 0) <= (others => '1');
            i(k) <= '0';
            wait for 1 ps;
        end loop;
    end process;
```

Timing Diagram

