

VLSI Lab Report Assignment 2

Annexure 2

BCSE 4th Year 2nd Semester

*Name: **Priti Shaw***

*Roll No. : **001710501076***


*Batch: **A3***

1. Design 16X4 Encoder using function and procedure.

Description

An encoder in digital electronics is a one-hot to binary converter. That is if there are $2n$ input lines, and at most only one of them will ever be high, the binary code of this 'hot' line is produced on the n -bit output lines. A 16-to-4 encoder has 16 input lines and 4 output line.


Block Diagram

 

Entity

```
entity 16X4_Encoder is
    Port ( ii : in  STD_LOGIC_VECTOR (15 downto 0);
          oo : out  STD_LOGIC_VECTOR (3  downto 0));
end Function_16X4_Encoder;
```

Circuit Diagram

 

Architecture

a) Using function of 4X2 encoders only

```
architecture Behavioral of Function_16X4_Encoder is
function Encoder_4X2_function(i:std_logic_vector)return std_logic_vector;

function Encoder_4X2_function(i:std_logic_vector)return std_logic_vector is
variable a:std_logic_vector(1 downto 0);
begin
    if i="0001" then
        a:="00";
```

```

        elsif i="0010" then
            a:="01";
        elsif i="0100" then
            a:="10";
        elsif i="1000" then
            a:="11";
        else
            a:="ZZ";
        end if;
    return a;
end function;

begin
process(ii)
    variable p:std_logic_vector(3 downto 0);
    variable k,j:integer;
    variable y:std_logic_vector(9 downto 0);
    begin
        for k in 0 to 3 loop
            p(k):='0';
            for j in 0 to 3 loop
                p(k):=p(k) or ii(4*k+j);
            end loop;
            y(2*k+1 downto 2*k):=Encoder_4X2_function(ii(4*k+3 downto
4*k));

            end loop;
            y(9 downto 8):=Encoder_4X2_function(p);
            if y(9 downto 8)="ZZ" then
                oo<="ZZZZ";
            else
                for k in 0 to 3 loop
                    if p(k)='1' then
                        if y(2*k+1 downto 2*k)="ZZ" then
                            oo<="ZZZZ";
                        else
                            oo<=y(9 downto 8) & y(2*k+1 downto
2*k);

                                end if;
                            end if;
                        end loop;
                    end if;
                end process;
end Behavioral;

```

b) Using procedure of 4X2 encoders only

```
architecture Behavioral of Procedure_16X4_Encoder is

    procedure Encoder_4X2_procedure(i:in std_logic_vector;o:out
    std_logic_vector);

    procedure Encoder_4X2_procedure(i:in std_logic_vector;o:out
    std_logic_vector) is
    begin
        if i="0001" then
            o:="00";
        elsif i="0010" then
            o:="01";
        elsif i="0100" then
            o:="10";
        elsif i="1000" then
            o:="11";
        else
            o:="ZZ";
        end if;
    end procedure;

begin
    process(ii)
        variable p:std_logic_vector(3 downto 0);
        variable k,j:integer;
        variable y:std_logic_vector(9 downto 0);
        begin
            for k in 0 to 3 loop
                p(k):='0';
                for j in 0 to 3 loop
                    p(k):=p(k) or ii(4*k+j);
                end loop;
                Encoder_4X2_procedure(ii(4*k+3 downto 4*k),y(2*k+1 downto
2*k));
            end loop;
            Encoder_4X2_procedure(p,y(9 downto 8));
            if y(9 downto 8)="ZZ" then
                oo<="ZZZZ";
            else
                for k in 0 to 3 loop
```

```

        if p(k)='1' then
            if y(2*k+1 downto 2*k)="ZZ" then
                oo<="ZZZZ";
            else
                oo<=y(9 downto 8) & y(2*k+1 downto 2*k);
            end if;
        end if;
    end loop;
end if;
end process;
end Behavioral;

```

TestBench

```

ENTITY Function_16X4_Encoder_TestBench IS
END Function_16X4_Encoder_TestBench;

ARCHITECTURE behavior OF Function_16X4_Encoder_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT Function_16X4_Encoder
    PORT(
        ii : IN  std_logic_vector(15 downto 0);
        oo : OUT std_logic_vector(3  downto 0)
    );
    END COMPONENT;

    --Inputs
    signal ii : std_logic_vector(15 downto 0) := (others => '0');
    --Outputs
    signal oo : std_logic_vector(3  downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: Function_16X4_Encoder PORT MAP (
        ii => ii,
        oo => oo
    );

    -- Stimulus process
    stim_proc: process
        variable a,k:integer;
    begin

```

```

    for k in 0 to 15 loop
        for a in 0 to 15 loop
            ii(a)<='0';
        end loop;
        ii(k)<='1';
        wait for 1 ps;
    end loop;
    ii<=(others=>'0');
    ii(0)<='1';
    ii(1)<='1';
    wait for 1 ps;
    ii<=(others=>'0');
    ii(0)<='1';
    ii(15)<='1';
    wait for 1 ps;
end process;
END;

```

Timing Diagram

a) Using function of 4X2 encoders only



b) Using procedure of 4X2 encoders only

