

VLSI Lab Report Assignment 1

BCSE 4th Year 2nd Semester

Name : Priti Shaw

Roll No. : 001710501076

Batch : A3

Submission Date : 13th March 2021

1. Description

Write VHDL code for two binary inputs *a* and *b* which outputs a bus of an 8-bit, *c* where each bit represents the following:

Bit	Represents
7	$c(7) \Rightarrow a \text{ AND } b$
6	$c(6) \Rightarrow a \text{ OR } b$
5	$c(5) \Rightarrow \text{NOT } a$
4	$c(4) \Rightarrow \text{NOT } b$
3	$c(3) \Rightarrow a \text{ NAND } b$
2	$c(2) \Rightarrow a \text{ NOR } b$
1	$c(1) \Rightarrow a \text{ XOR } b$
0	$c(0) \Rightarrow a \text{ XNOR } b$


Also, verify the result by using testbench and plot the timing diagram.

2. Entity



Inputs: a, b
Output: c

3. Logic Gate

 

4. Truth Table

Input		Output							
a	b	c							
		7	6	5	4	3	2	1	0
0	0	0	0	1	1	1	1	0	1
0	1	0	1	1	0	1	0	1	0
1	0	0	1	0	1	1	0	1	0
1	1	1	1	0	0	0	0	0	1

5. Architecture

```
-----  
-- Company:  
-- Engineer:  
--  
-- Create Date:    18:20:17 03/10/2021  
-- Design Name:  
-- Module Name:    Logic_Gates - Behavioral  
-- Project Name:  
-- Target Devices:  
-- Tool versions:  
-- Description:  
--  
-- Dependencies:  
--  
-- Revision:  
-- Revision 0.01 - File Created  
-- Additional Comments:  
--  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
-- Uncomment the following library declaration if using  
-- arithmetic functions with Signed or Unsigned values  
--use IEEE.NUMERIC_STD.ALL;  
  
-- Uncomment the following library declaration if instantiating  
-- any Xilinx primitives in this code.  
--library UNISIM;  
--use UNISIM.VComponents.all;  
  
entity Logic_Gates is  
    Port ( a : in  STD_LOGIC;  
          b : in  STD_LOGIC;  
          c : out STD_LOGIC_VECTOR (7 downto 0));  
end Logic_Gates;  
  
architecture Behavioral of Logic_Gates is  
  
begin  
    c(7) <= a and b;  
    c(6) <= a or b;  
    c(5) <= not a;  
    c(4) <= not b;  
    c(3) <= a nand b;  
    c(2) <= a nor b;  
    c(1) <= a xor b;  
    c(0) <= a xnor b;  
end Behavioral;
```

6. Test Bench

```
-----
-- Company:
-- Engineer:
--
-- Create Date:   18:33:44 03/10/2021
-- Design Name:
-- Module Name:   /mnt/e/JU/8/VLSI/Lab/Code/Assignment1/Logic_Gates_Test_Bench.vhd
-- Project Name:  Assignment1
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: Logic_Gates
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
-----
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY Logic_Gates_Test_Bench IS
END Logic_Gates_Test_Bench;

ARCHITECTURE behavior OF Logic_Gates_Test_Bench IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Logic_Gates
    PORT(
        a : IN  std_logic;
        b : IN  std_logic;
        c : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;


```

```

--Inputs
signal aa : std_logic := '0';
signal bb : std_logic := '0';

--Outputs
signal cc : std_logic_vector(7 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Logic_Gates PORT MAP (
        a => aa,
        b => bb,
        c => cc
    );

    -- Stimulus process
    stim_proc: process
    begin
        aa <= '0';
        bb <= '0';
        wait for 1 ps;

        aa <= '0';
        bb <= '1';
        wait for 1 ps;

        aa <= '1';
        bb <= '0';
        wait for 1 ps;

        aa <= '1';
        bb <= '1';
        wait for 1 ps;

    end process;
END;

```

7. Timing Diagram

