

# **VLSI Lab Report Assignment 3**

## **Annexure 2**

**BCSE 4th Year 2nd Semester**

*Name: **Priti Shaw***

*Roll No. : **001710501076***


*Batch: **A3***

# 1. Design 4X16 Decoder using function and procedure.

## Description

A decoder is a combinational circuit that has N input lines and a maximum of  $2^N$  output lines. One of these outputs will be active high based on the combination of inputs present when the decoder is enabled. That means the decoder detects a particular code. A 1 to 2 decoder has 1 input line and 2 output lines. An enable input is provided to switch the decoder on and off.


## Block Diagram

 

## Entity

```
entity 4X16_Decoder is
    Port ( ii : in  STD_LOGIC_VECTOR (3 downto 0);
          oo : out  STD_LOGIC_VECTOR (15 downto 0);
          ee : in  STD_LOGIC);
end Function_4X16_Decoder;
```

## Circuit Diagram

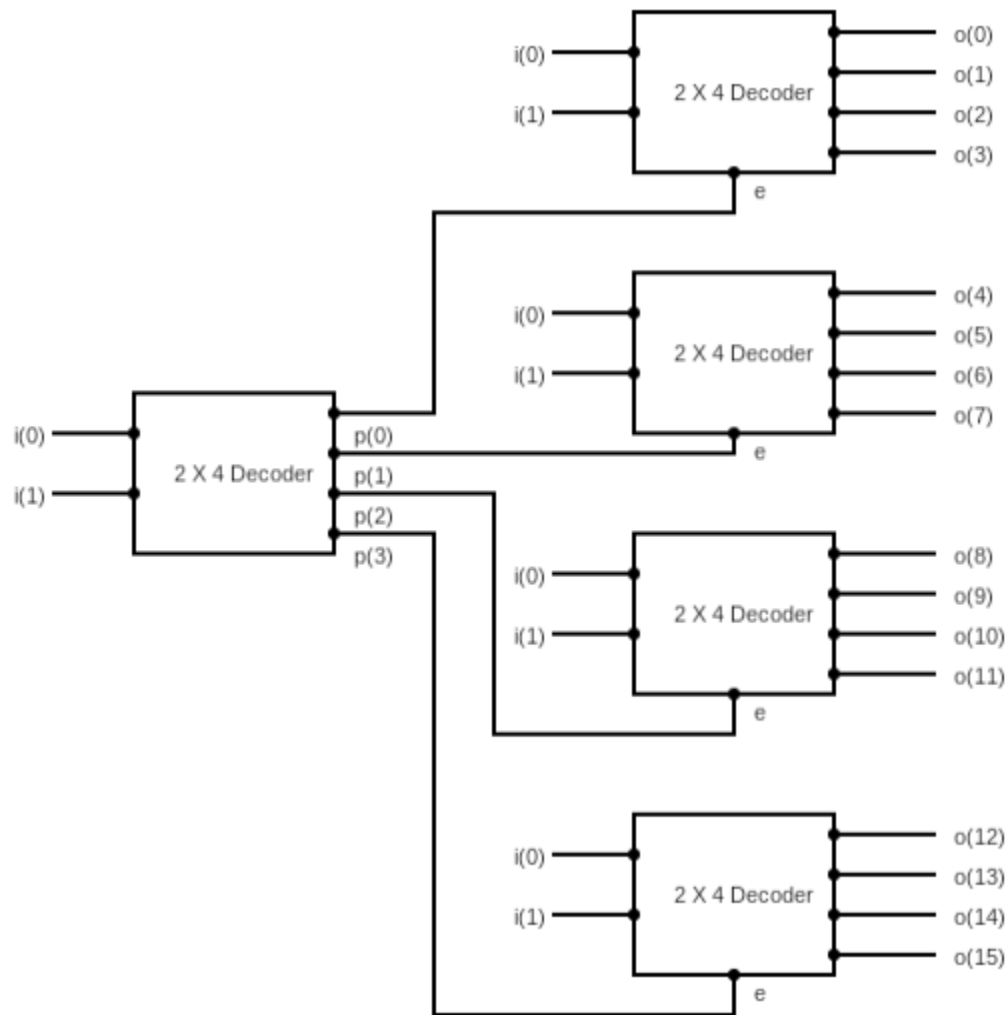

## Architecture

a) Using function of 2X4 decoders only

```
architecture Behavioral of Function_4X16_Decoder is
```

```
function Decoder_2X4_function(i:in std_logic_vector;e:in std_logic)return  
std_logic_vector;
```

```
function Decoder_2X4_function(i:in std_logic_vector;e:in std_logic)return  
std_logic_vector is
```

```
    variable a:std_logic_vector(3 downto 0);
```

```
    begin
```

```
    if e='0' then
```

```

        a:="0000";
    elsif e='1' then
        if i="00" then
            a:="0001";
        elsif i="01" then
            a:="0010";
        elsif i="10" then
            a:="0100";
        elsif i="11" then
            a:="1000";
        end if;
    end if;
    return a;
end function;

begin
process(ii,ee)
variable p:std_logic_vector(3 downto 0);
variable k:integer;
variable y:std_logic_vector(15 downto 0);
    begin
        p:=Decoder_2X4_function(ii(3 downto 2),ee);
        for k in 0 to 3 loop
            y(4*k+3 downto 4*k):=Decoder_2X4_function(ii(1 downto 0),p(k));
        end loop;
        oo<=y;
    end process;
end Behavioral;

```

## b) Using procedure of 2X4 decoders only

```

architecture Behavioral of Procedure_4X16_Decoder is

    procedure Decoder_2X4_procedure(i:in std_logic_vector;e:in std_logic;o:out
std_logic_vector);

    procedure Decoder_2X4_procedure(i:in std_logic_vector;e:in std_logic;o:out
std_logic_vector) is
        begin
            if e='0' then
                o:="0000";
            end if;
        end Decoder_2X4_procedure;
    end Decoder_2X4_procedure;

end architecture Behavioral;

```

```

        elsif e='1' then
            if i="00" then
                o:="0001";
            elsif i="01" then
                o:="0010";
            elsif i="10" then
                o:="0100";
            elsif i="11" then
                o:="1000";
            end if;
        end if;
    end procedure;

begin
    process(ii,ee)
        variable p:std_logic_vector(3 downto 0);
        variable k:integer;
        variable y:std_logic_vector(15 downto 0);
        begin
            Decoder_2X4_procedure(ii(3 downto 2),ee,p);
            for k in 0 to 3 loop
                Decoder_2X4_procedure(ii(1 downto 0),p(k),y(4*k+3 downto
4*k));
            end loop;
            oo<=y;
        end process;
    end Behavioral;

```

## TestBench

```

ENTITY Function_4X16_Decoder_TestBench IS
END Function_4X16_Decoder_TestBench;

ARCHITECTURE behavior OF Function_4X16_Decoder_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT Function_4X16_Decoder
    PORT(
        ii : IN  std_logic_vector(3 downto 0);
        oo : OUT std_logic_vector(15 downto 0);
        ee : IN  std_logic

```

```

    );
END COMPONENT;

--Inputs
signal ii : std_logic_vector(3 downto 0) := (others => '0');
signal ee : std_logic := '0';
--Outputs
signal oo : std_logic_vector(15 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Function_4X16_Decoder PORT MAP (
        ii => ii,
        oo => oo,
        ee => ee
    );

    -- Stimulus process
    stim_proc: process
        variable k,j,a:integer;
        begin
            if ee='0' then
                ee<='1';
            elsif ee='1' then
                ee<='0';
            end if;
            for k in 0 to 15 loop
                j:=k;
                a:=0;
                while a<4 loop
                    if (j rem 2)=0 then
                        ii(a)<='0';
                    elsif (j rem 2)=1 then
                        ii(a)<='1';
                    end if;
                    j:=j/2;
                    a:=a+1;
                end loop;
                wait for 1 ps;
            end loop;
        end process;
END;
```

# Timing Diagram

a) Using function of 2X4 decoders only



b) Using procedure of 2X4 decoders only

