

VLSI Lab Report Assignment 3

BCSE 4th Year 2nd Semester

*Name: **Priti Shaw***

*Roll No. : **001710501076***

*Batch: **A3***

1. Design 1 X 2 Decoder

Description


Design 1 X 2 decoder using gate and behavioral level modeling.

A decoder is a combinational circuit that has N input lines and a maximum of 2^N output lines. One of these outputs will be active high based on the combination of inputs present when the decoder is enabled. That means the decoder detects a particular code. A 1 to 2 decoder has 1 input line and 2 output lines. An enable input is provided to switch the decoder on and off.


Truth Table

Input		Output	
e	i ₀	o ₁	o ₀
0	X	X	X
1	0	0	1
1	1	1	0

Block Diagram

 

Circuit Diagram

 

Entity

```
entity QuestionOne is
    Port ( e : in  STD_LOGIC;
           i : in  STD_LOGIC;
           o : out  STD_LOGIC_VECTOR (1 downto 0));
end QuestionOne;
```

Architecture

a) Using **gate-level** modeling

```
architecture Behavioral of QuestionOne_PartA is

begin
    o(0) <= e and not(i);
    o(1) <= e and i;
end Behavioral;
```

b) Using **behavioral-level** modeling

i. Using **if-else** statement

```
architecture Behavioral of QuestionOne_PartB_One is

begin
    p1:process(e, i)
    begin
        if e='0' then
```

```

        o<="00";
    elsif i='0' then
        o<="01";
    elsif i='1' then
        o<="10";
    end if;
end process;
end Behavioral;

```

ii. Using **case** statement

```

architecture Behavioral of QuestionOne_PartB_two is

begin
p2:process(e,i)
    begin
        case e is
            when '0' => o<="00";
            when '1' =>
                case i is
                    when '0' => o<="01";
                    when '1' => o<="10";
                    when others => o<="ZZ";
                end case;
            when others => o<="ZZ";
        end case;
    end process;
end Behavioral;

```

iii. Using **when else** statement

```

architecture Behavioral of QuestionOne_PartB_three is

begin
o<="00" when e<='0' else
    "01" when i<='0' else
    "10" when i<='1' else
    "ZZ";
end Behavioral;

```

iv. Using **switch** when statement

```
architecture Behavioral of QuestionOne_PartB_four is

begin
    with (e&i) select
        o <= "01" when "10",
            "10" when "11",
            "00" when "00",
            "ZZ" when others;

end Behavioral;
```

TestBench

```
ENTITY QuestionOne_Testbench IS
END QuestionOne_Testbench;

ARCHITECTURE behavior OF QuestionOne_Testbench IS
    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT QuestionOne
    PORT(
        e : IN  std_logic;
        i : IN  std_logic;
        o : OUT std_logic_vector(1 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal e : std_logic := '0';
    signal i : std_logic := '0';
    --Outputs
    signal o : std_logic_vector(1 downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionOne_PartB_four PORT MAP (
        e => e,
        i => i,
        o => o
    );

    -- Stimulus process
    stim_proc: process
```

```

begin
    e<='0';
    i<='0';
    wait for 1 ps;
    e<='1';
    i<='0';
    wait for 1 ps;
    i<='1';
    wait for 1 ps;
end process;
END;

```


Timing Diagram

a) Using **gate-level** modeling




b) Using **behavioral-level** modeling


i) Using **if-else** statement

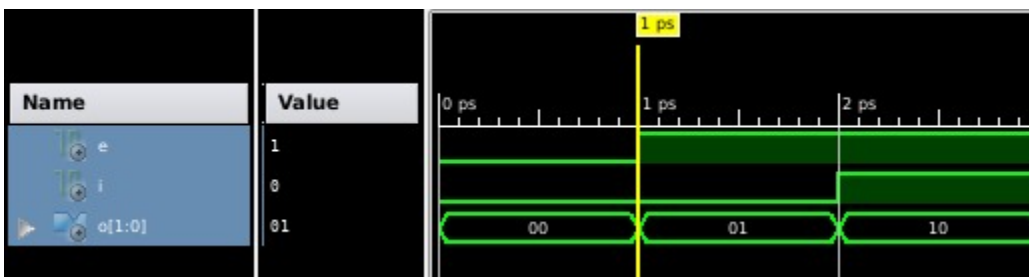

ii) Using **case** statement

 

iii) Using **when else** statement

 

iv) Using **select when** statement



2. Design 2 X 4 Decoder

Description


Design 2 X 4 decoder using gate and behavioral level modeling.

A decoder is a combinational circuit that has N input lines and a maximum of 2^N output lines. A 2 to 4 decoder has 2 input lines and 4 output lines. An enable input is provided to switch the decoder on and off.


Truth Table

Input			Output			
e	i ₁	i ₀	o ₃	o ₂	o ₁	o ₀
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Block Diagram

 

Circuit Diagram

 

Entity

```
entity QuestionTwo is
  Port ( e : in  STD_LOGIC;
         ii : in  STD_LOGIC_VECTOR (1 downto 0);
         oo : out STD_LOGIC_VECTOR (3 downto 0));
end QuestionTwo;
```

Architecture

a) Using **gate-level** modeling

```
architecture Behavioral of QuestionTwo_PartA is
```



```

begin
    oo(0)<= e and not(ii(1)) and not(ii(0));
    oo(1)<= e and not(ii(1)) and ii(0);
    oo(2)<= e and (ii(1)) and not(ii(0));
    oo(3)<= e and (ii(1)) and ii(0);
end Behavioral;

```

b) Using *behavioral-level* modeling

i. Using **if-else** statement

```

architecture Behavioral of QuestionTwo_PartB_one is

begin
p1:process(ee, ii)
    begin
        if ee='0' then
            oo<="0000";
        elsif ii="00" then
            oo<="0001";
        elsif ii="01" then
            oo<="0010";
        elsif ii="10" then
            oo<="0100";
        elsif ii="11" then
            oo<="1000";
        else
            oo<="ZZZZ";
        end if;
    end process;
end Behavioral;

```

ii. Using **case** statement

```

architecture Behavioral of QuestionOne_PartB_two is

begin
p2:process(e,i)
    begin
        case e is
            when '0' => o<="00";
            when '1' =>

```

```

        case i is
            when '0' => o<="01";
            when '1' => o<="10";
            when others => o<="ZZ";
        end case;
        when others => o<="ZZ";
    end case;
end process;
end Behavioral;

```

iii. Using **when else** statement

```

architecture Behavioral of QuestionTwo_PartB_three is

begin
oo<="0000" when e<='0' else
    "0001" when ii<="00" else
    "0010" when ii<="01" else
    "0100" when ii<="10" else
    "1000" when ii<="11" else
    "ZZZZ";
end Behavioral;

```

iv. Using **switch** when statement

```

architecture Behavioral of QuestionTwo_PartB_Four is

begin
with (e&ii) select
    oo <= "0001" when "100",
           "0010" when "101",
           "0100" when "110",
           "1000" when "111",
           "0000" when others;
end Behavioral;

```

TestBench

```

ENTITY QuestionTwo_TestBench IS
END QuestionTwo_TestBench;

```

```

ARCHITECTURE behavior OF QuestionTwo_TestBench IS
    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT QuestionTwo_PartB_Four
    PORT(
        e : IN  std_logic;
        ii : IN  std_logic_vector(1 downto 0);
        oo : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal e : std_logic := '0';
    signal ii : std_logic_vector(1 downto 0) := (others => '0');

    --Outputs
    signal oo : std_logic_vector(3 downto 0);


BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionTwo_PartB_Four PORT MAP (
        e => e,
        ii => ii,
        oo => oo
    );

    -- Stimulus process
    stim_proc: process
    begin
        e<='0';
        ii<="00";
        wait for 1 ps;
        e<='1';
        ii<="00";
        wait for 1 ps;
        ii<="01";
        wait for 1 ps;
        ii<="10";
        wait for 1 ps;
        ii<="11";
        wait for 1 ps;
    end process;
END;

```


Timing Diagram

a) Using **gate-level** modeling

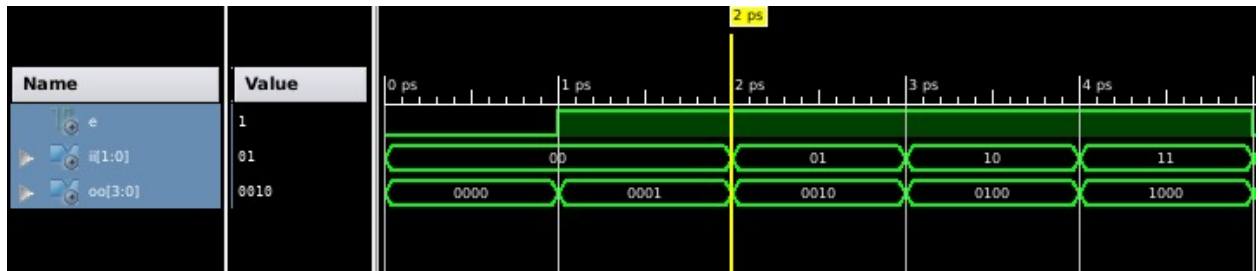


b) Using **behavioral-level** modeling


i) Using **if-else** statement

 


ii) Using **case** statement

 

iii) Using **when else** statement

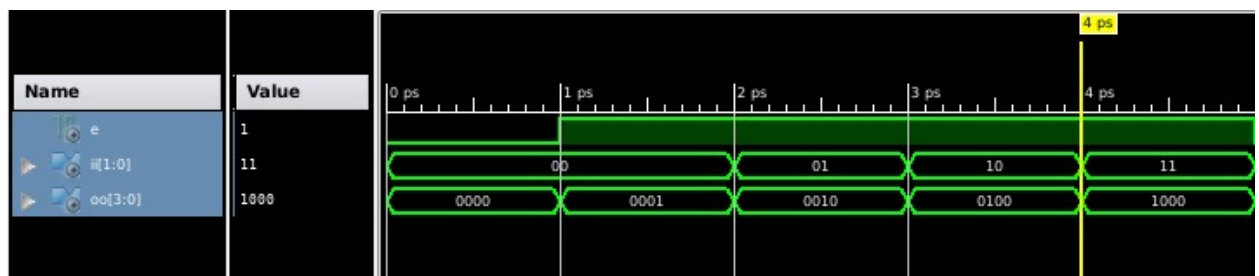

iv) Using **select when** statement

 


3. Design 3 X 8 Decoder

Description

Design 3 X 8 decoder using gate and behavioral level modeling.

A decoder is a combinational circuit that has N input lines and a maximum of 2^N output lines. One of these outputs will be active high based on the combination of inputs present when the decoder is enabled. That means the decoder detects a particular code. A 3 to 8 decoder has 3 input lines and 8 output lines. An enable input is provided to switch the decoder on and off.


Block Diagram

 

Truth Table

Input				Output							
e	i ₂	i ₁	i ₀	o ₇	o ₆	o ₅	o ₄	o ₃	o ₂	o ₁	o ₀
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Circuit Diagram

 

Entity

```
entity QuestionThree is
    Port ( e : in  STD_LOGIC;
           iii : in  STD_LOGIC_VECTOR (2 downto 0);
```

```
ooo : out STD_LOGIC_VECTOR (7 downto 0));  
end QuestionThree;
```

Architecture

a) Using **gate-level** modeling

```
architecture Behavioral of QuestionThree_PartA is  
  
begin  
ooo(7)<= e and iii(2) and iii(1) and iii(0);  
ooo(6)<= e and iii(2) and iii(1) and (not(iii(0)));  
ooo(5)<= e and iii(2) and iii(0) and not(iii(1));  
ooo(4)<= e and iii(2) and (iii(1) nor iii(0));  
ooo(3)<= e and iii(1) and iii(0) and (not iii(2));  
ooo(2)<= e and iii(1) and (iii(2) nor iii(0));  
ooo(1)<= e and iii(0) and (iii(2) nor iii(1));  
ooo(0)<= e and not(iii(0) or iii(1) or iii(2));  
end Behavioral;
```

b) Using **behavioral-level** modeling

i. Using **if-else** statement

```
architecture Behavioral of QuestionThree_PartB_one is  
  
begin  
p1:process(e, iii)  
begin  
if e='0' then  
ooo<="00000000";  
elsif iii="000" then  
ooo<="00000001";  
elsif iii="001" then  
ooo<="00000010";  
elsif iii="010" then  
ooo<="00000100";  
elsif iii="011" then  
ooo<="00001000";  
elsif iii="100" then
```

```

        ooo<="00010000";
    elsif iii="101" then
        ooo<="00100000";
    elsif iii="110" then
        ooo<="01000000";
    elsif iii="111" then
        ooo<="10000000";
    end if;
end process;
end Behavioral;

```

ii. Using **case** statement

```

architecture Behavioral of QuestionThree_PartB_two is

begin
    p2:process(e,iii)
    begin
        case e is
            when '0' => ooo<="00000000";
            when '1' =>
                case iii is
                    when "000" => ooo<="00000001";
                    when "001" => ooo<="00000010";
                    when "010" => ooo<="00000100";
                    when "011" => ooo<="00001000";
                    when "100" => ooo<="00010000";
                    when "101" => ooo<="00100000";
                    when "110" => ooo<="01000000";
                    when "111" => ooo<="10000000";
                    when others => ooo<="ZZZZZZZZ";
                end case;
            when others => ooo<="ZZZZZZZZ";
        end case;
    end process;
end Behavioral;

```

iii. Using **when else** statement

```

architecture Behavioral of QuestionThree_PartB_three is

begin

```



```

ooo<="00000000" when e<='0' else
    "00000001" when iii<="000" else
    "00000010" when iii<="001" else
    "00000100" when iii<="010" else
    "00001000" when iii<="011" else
    "00010000" when iii<="100" else
    "00100000" when iii<="101" else
    "01000000" when iii<="110" else
    "10000000" when iii<="111" else
    "ZZZZZZZZ";
end Behavioral;

```

iv. Using **switch** when statement

```

architecture Behavioral of QuestionThree_PartB_four is

begin
with (e&iii) select
    ooo <= "00000001" when "1000",
           "00000010" when "1001",
           "00000100" when "1010",
           "00001000" when "1011",
           "00010000" when "1100",
           "00100000" when "1101",
           "01000000" when "1110",
           "10000000" when "1111",
           "00000000" when others;
end Behavioral;

```

TestBench

```

ENTITY QuestionThree_Testbench IS
END QuestionThree_Testbench;

ARCHITECTURE behavior OF QuestionThree_Testbench IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT QuestionThree_PartB_one
    PORT(
        e : IN  std_logic;

```

```

        iii : IN  std_logic_vector(2 downto 0);
        ooo : OUT std_logic_vector(7 downto 0)
    );
END COMPONENT;

--Inputs
signal e : std_logic := '0';
signal iii : std_logic_vector(2 downto 0) := (others => '0');

--Outputs
signal ooo : std_logic_vector(7 downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionThree_PartB_one PORT MAP (
        e => e,
        iii => iii,
        ooo => ooo
    );
    -- Stimulus process
    stim_proc: process
    begin
        e<='0';
        iii<="000";
        wait for 1 ps;
        e<='1';
        iii<="000";
        wait for 1 ps;
        iii<="001";
        wait for 1 ps;
        iii<="010";
        wait for 1 ps;
        iii<="011";
        wait for 1 ps;
        iii<="100";
        wait for 1 ps;
        iii<="101";
        wait for 1 ps;
        iii<="110";
        wait for 1 ps;
        iii<="111";
        wait for 1 ps;
    end process;


```

```
end process;

END;
```


Timing Diagram

a) Using **gate-level** modeling

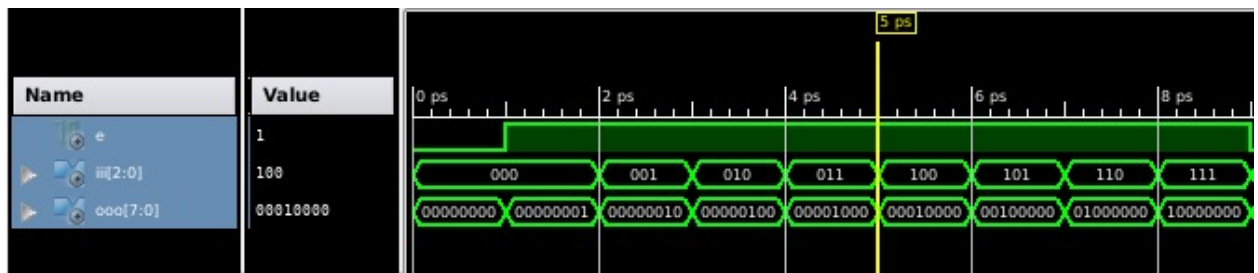


b) Using **behavioral-level** modeling


i) Using **if-else** statement

 


ii) Using **case** statement

 

iii) Using **when else** statement

 

iv) Using **select when** statement

 


4. Design 3 X 8 Decoder using Component Instantiation.

Description

Design 3 X 8 decoder using 2 X 4 decoder and 1 X 2 decoder by component instantiation.

A 3 to 8 decoder has 3 input lines and 8 output lines. An enable input is provided to switch the decoder on and off.


Block Diagram

 

Truth Table

Input				Output							
e	i ₂	i ₁	i ₀	o ₇	o ₆	o ₅	o ₄	o ₃	o ₂	o ₁	o ₀
0	X	X	X	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Circuit Diagram

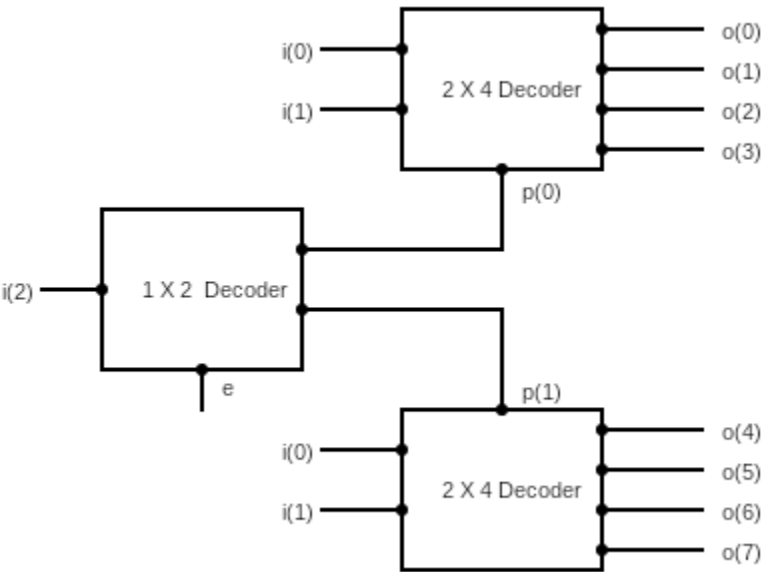

Entity

```
entity QuestionFour is
    Port ( eee : in  STD_LOGIC;
           iii : in  STD_LOGIC_VECTOR (2 downto 0);
           ooo : out STD_LOGIC_VECTOR (7 downto 0));
end QuestionFour;
```

Architecture

```
architecture Behavioral of QuestionFour is

    -- 2 X 4 Decoder
    component QuestionTwo_PartB_one is
        Port ( ee : in  STD_LOGIC;
              ii : in  STD_LOGIC_VECTOR (1 downto 0);
              oo : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    -- 1 X 2 Decoder
    component QuestionOne_PartB_One is
        Port ( e : in  STD_LOGIC;
              i : in  STD_LOGIC;
              o : out STD_LOGIC_VECTOR (1 downto 0));
    end component;
    signal p: STD_LOGIC_VECTOR(1 downto 0);

begin
    c1: QuestionTwo_PartB_one port map(p(0), iii(1 downto 0), oooo(3 downto 0));
    c2: QuestionTwo_PartB_one port map(p(1), iii(1 downto 0), oooo(7 downto 4));
    c3: QuestionOne_PartB_One port map(eeee, iii(2), p);
end Behavioral;
```

TestBench

```
ENTITY QuestionFive_TestBench IS
END QuestionFive_TestBench;

ARCHITECTURE behavior OF QuestionFive_TestBench IS
```

```

-- Component Declaration for the Unit Under Test (UUT)
COMPONENT QuestionFive
PORT(
    eeeee : IN  std_logic;
    iiii : IN  std_logic_vector(3 downto 0);
    oooo : OUT  std_logic_vector(15 downto 0)
);
END COMPONENT;

--Inputs
signal eeeee : std_logic := '0';
signal iiii : std_logic_vector(3 downto 0) := (others => '0');

--Outputs
signal oooo : std_logic_vector(15 downto 0);

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: QuestionFive PORT MAP (
        eeeee => eeeee,
        iiii => iiii,
        oooo => oooo
    );
    -- Stimulus process
    stim_proc: process
    begin
        eeeee<='0';
        iiii<="0000";
        wait for 1 ps;
        eeeee<='1';
        iiii<="0000";
        wait for 1 ps;
        iiii<="0001";
        wait for 1 ps;
        iiii<="0010";
        wait for 1 ps;
        iiii<="0011";
        wait for 1 ps;
        iiii<="0100";
        wait for 1 ps;
        iiii<="0101";
        wait for 1 ps;
        iiii<="0110";
    end process;
end


```

```

wait for 1 ps;
iiii<="0111";
wait for 1 ps;
iiii<="1000";
wait for 1 ps;
iiii<="1001";
wait for 1 ps;
iiii<="1010";
wait for 1 ps;
iiii<="1011";
wait for 1 ps;
iiii<="1100";
wait for 1 ps;
iiii<="1101";
wait for 1 ps;
iiii<="1110";
wait for 1 ps;
iiii<="1111";
wait for 1 ps;
end process;
END;

```

Timing Diagram

 


5. Design 4 X 16 Decoder using Component Instantiation.

Description

Design 4 X 16 decoder using 2 X 4 decoder by component instantiation.

A decoder is a combinational circuit that has N input lines and a maximum of 2^N output lines. One of these outputs will be active high based on the combination of inputs present when the decoder is enabled. That means the decoder detects a particular code. A 4 to 16 decoder has 4 input lines and 16 output lines. An enable input is provided to switch the decoder on and off.


Block Diagram

 

Truth Table

[illegible]

Circuit Diagram

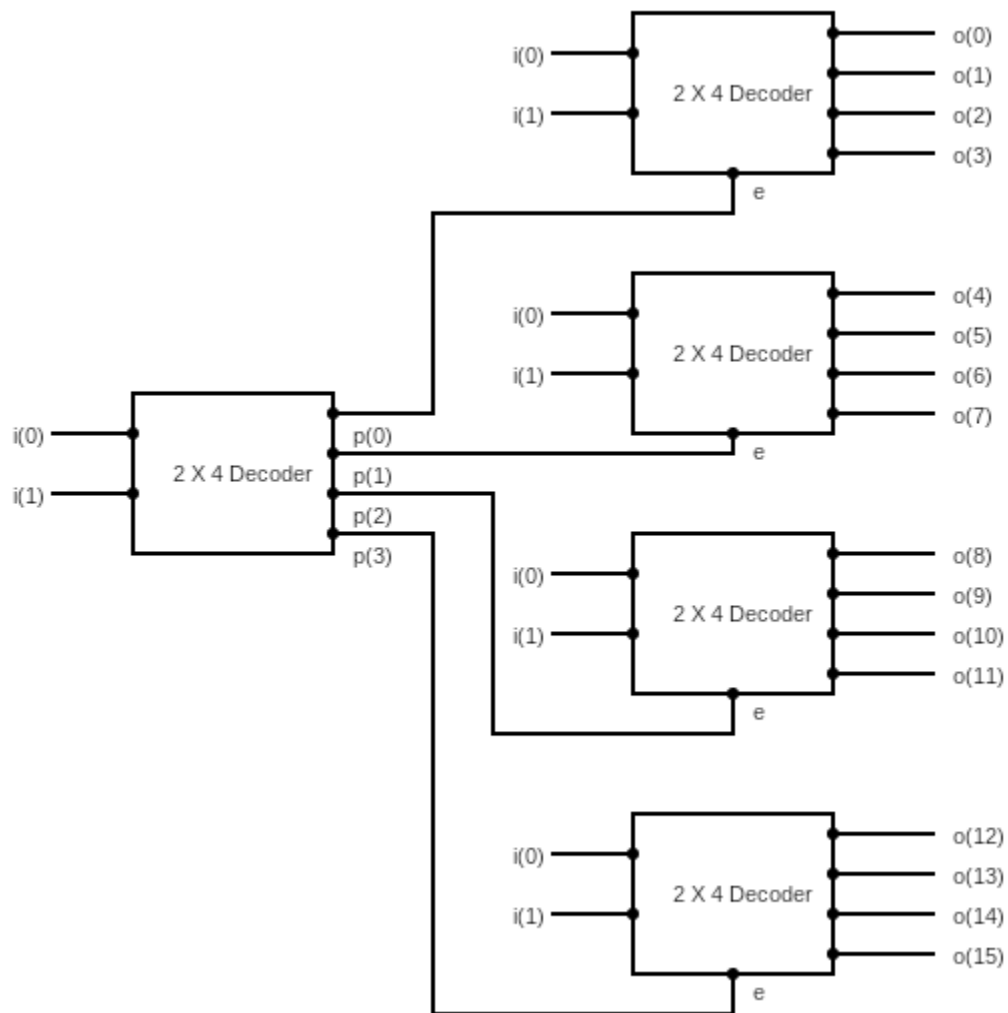

Entity

```
entity QuestionFive is
    Port ( eeee : in  STD_LOGIC;
          iiii : in  STD_LOGIC_VECTOR (3 downto 0);
          oooo : out STD_LOGIC_VECTOR (15 downto 0));
end QuestionFive;
```

Architecture

```
architecture Behavioral of QuestionFive is

component QuestionTwo_PartB_one is
    Port ( ee : in  STD_LOGIC;
          ii : in  STD_LOGIC_VECTOR (1 downto 0);
          oo : out STD_LOGIC_VECTOR (3 downto 0));
end component;

signal p: STD_LOGIC_VECTOR(3 downto 0);

begin
c1: QuestionTwo_PartB_one port map(p(0), iiii(1 downto 0), oooo(3 downto 0));
c2: QuestionTwo_PartB_one port map(p(1), iiii(1 downto 0), oooo(7 downto 4));
c3: QuestionTwo_PartB_one port map(p(2), iiii(1 downto 0), oooo(11 downto 8));
c4: QuestionTwo_PartB_one port map(p(3), iiii(1 downto 0), oooo(15 downto 12));
c5: QuestionTwo_PartB_one port map(eeeee, iiii(3 downto 2), p);

end Behavioral;
```

TestBench

```
ENTITY QuestionFive_TestBench IS
END QuestionFive_TestBench;

ARCHITECTURE behavior OF QuestionFive_TestBench IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT QuestionFive
    PORT(
        eeeee : IN  std_logic;
        iiii  : IN  std_logic_vector(3 downto 0);
        oooo  : OUT  std_logic_vector(15 downto 0)
    );
    END COMPONENT;
```

```
--Inputs
signal eeeee : std_logic := '0';
signal iiii : std_logic_vector(3 downto 0) := (others => '0');
--Outputs
signal oooo : std_logic_vector(15 downto 0);
```

```
BEGIN
```

```
    -- Instantiate the Unit Under Test (UUT)
```

```
    uut: QuestionFive PORT MAP (
        eeeee => eeeee,
        iiii => iiii,
        oooo => oooo
    );
```

```
    -- Stimulus process
```

```
    stim_proc: process
    begin
```

```
        eeeee<='0';
        iiii<="0000";
        wait for 1 ps;
        eeeee<='1';
        iiii<="0000";
        wait for 1 ps;
        iiii<="0001";
        wait for 1 ps;
        iiii<="0010";
        wait for 1 ps;
        iiii<="0011";
        wait for 1 ps;
        iiii<="0100";
        wait for 1 ps;
        iiii<="0101";
        wait for 1 ps;
        iiii<="0110";
        wait for 1 ps;
        iiii<="0111";
        wait for 1 ps;
        iiii<="1000";
        wait for 1 ps;
        iiii<="1001";
        wait for 1 ps;
        iiii<="1010";
        wait for 1 ps;
        iiii<="1011";
```

```

    wait for 1 ps;
    iiii<="1100";
    wait for 1 ps;
    iiii<="1101";
    wait for 1 ps;
    iiii<="1110";
    wait for 1 ps;
    iiii<="1111";
    wait for 1 ps;
end process;
END;

```

Timing Diagram

